

fig. [DC series motor]

Observation

Torque ( $T_1$ )	$T_2$	RPM (N)	Current (A)	Torque
0	0	1500	0.70	0
1	0.8	680	1.5	0.2
1.2	0.75	608	1.7	0.45
2	1	471	2.1	1
2.5	1.2	408	2.3	1.3
3.5	1	328	2.7	2.75
3.75	1.25	310	2.8	2.5

$$\text{Torque} = T_1 - T_2$$

N(RPM) is speed of motor

## Practical - 1

Aim - To Study the characteristics of DC series motor.

Equipment required - DC Series motor, Tachometer, Load belt, and Power Supply.

Theory - DC motor is a type of dc machines which convert electrical energy into mechanical energy. The operation of motor mainly depends on the electromagnetic principle.


Whenever magnetic field is founded approximately a current carrying conductor cooperates with a exterior magnetic field and then exerting motion can be generated.

In Series motor, field windings are in series with the rotating armature.


EMF equation

$$E_b = \frac{P\Phi Z N}{60A}$$

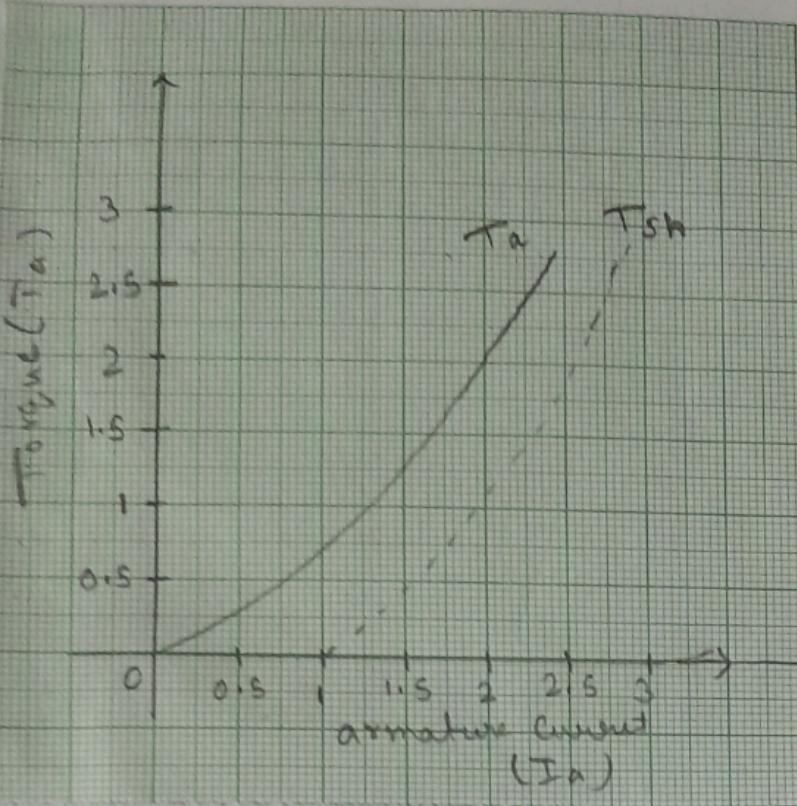
here,  $N \propto \frac{E_b}{\Phi}$  and  $T \propto \Phi \times I_a$



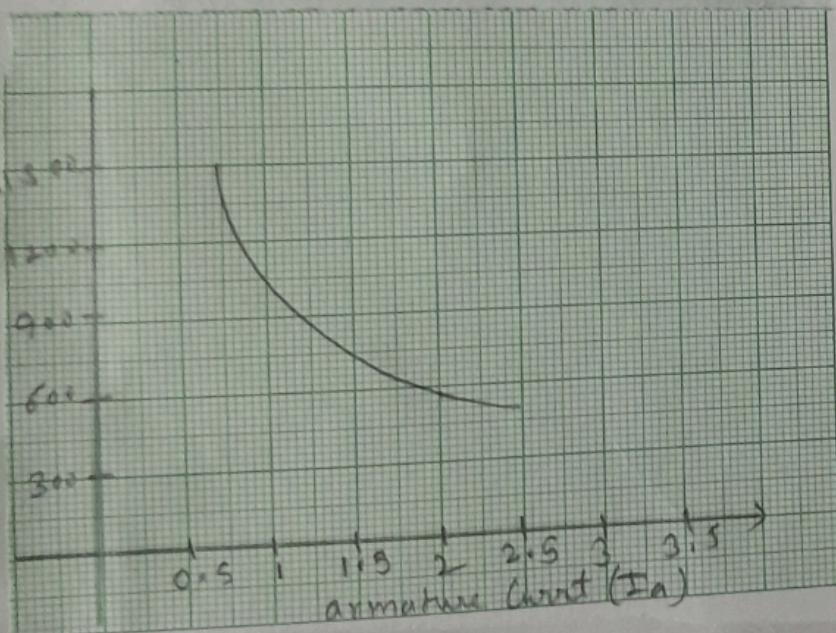Torque vs Armature Current  
( $T_a$  vs  $I_a$ )



( $N$  vs  $I_a$ )

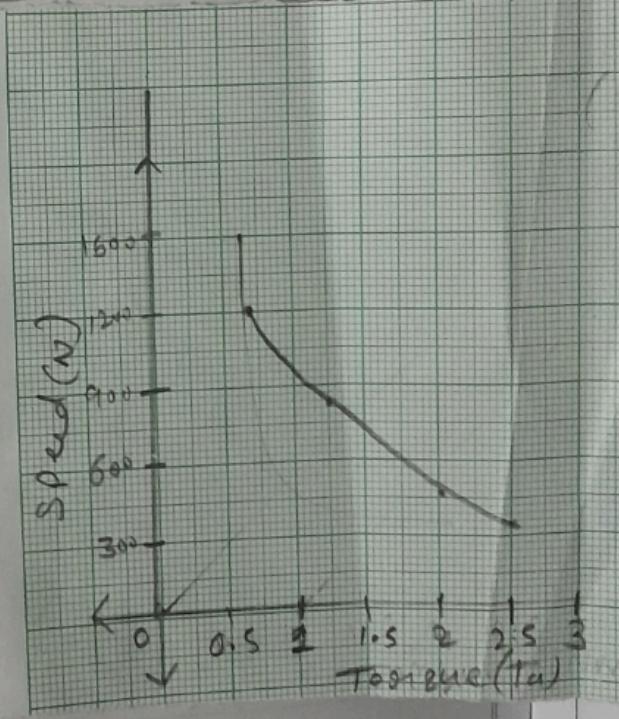

( $N$  vs  $T_a$ )

Expt. No. \_\_\_\_\_

Torque is directly proportional to Current & Speed inversely proportional to Current & Speed should be inversely proportional and so i/p Current.

### Result

Graph of  $T_a$  vs  $I_a$ ,  $N$  vs  $I_a$  and  $N$  vs  $T_a$  is successfully drawn.

### Precautions

- There should be load load while starting DC series motor
- Speed should not exceed max. limit.

## Observation table

Torque	Current	Speed
1.2	4.5	0
1.4	4.4	300
1.7	4.3	600
2.1	4.2	900
2.8	4.1	1200
3.8	3.9	1500
3.6	2	1650
3.3	3.7	1350
0	0.2	1800

Expt. No. \_\_\_\_\_

## Practical - 2

**Aim**  
To Study Characteristics of DC Series Single Phase Induction motor.

**Equipment Required**

Single phase Induction motor, Auto transformer, Tachometer,  
Ammeter.

**Theory**

Single phase induction motor are not self-starting motor. One method of them of self-starting is by providing windings on the. The motor rotor has proper three phase windings with three leads brought out ~~even~~ through slip rings and brushes. These leads are normally short circuited when the motor is running.

Resistance are introduced in a motor circuit via that slip rings at the time of starting to improve the starting torque.

Synchronous speed  $N_s$  is given by

$$N_s = \frac{120f}{P}$$

$f \rightarrow$  no. of Pole

Teacher's Signature : \_\_\_\_\_

Expt. No. \_\_\_\_\_

Result

The characteristics of single phase induction motor is  
successfully drawn

Precautions

- Before switching on the supply the Varisty is kept in minimum position
- Initially there should be no load while starting the motor.

Teacher's Signature : \_\_\_\_\_

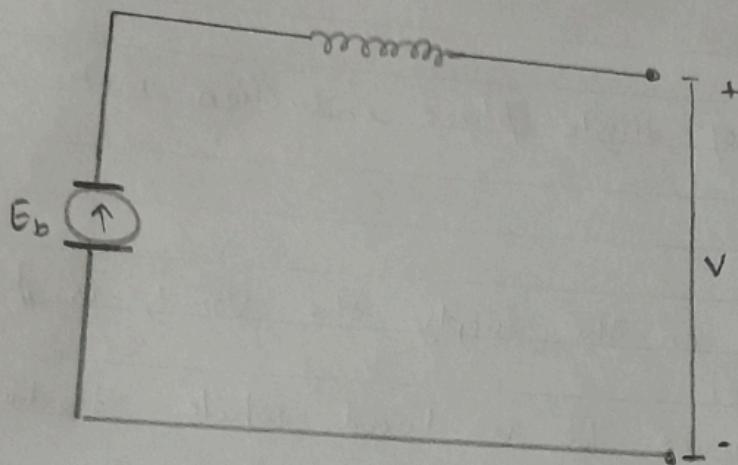


fig. (DC shunt motor)

### Observation

Torque $T_1$	Torque $T_2$	RPM(N)	Current(A)	Torque
0	0	1500	0.70	0
1	0.8	620	1.5	0.2
1.2	0.75	608	1.7	0.45
2	1	471	2.1	1
2.5	1.2	408	2.3	1.3
3.5	-1	328	2.2	2.75
3.75	1.25	310	2.1	2.5

### Practical - 3

#### Aim

To study the characteristics of a DC Shunt motor.

#### Equipment Required

DC Shunt motor, Tachometer, Load belt & Power Supply.

#### Theory

It is a type of dc <sup>wall</sup> motor which convert electrical energy into mechanical energy.

Whenever DC motor is turned on, then DC flows throughout the stator as well as the motor. This current flows will generate two fields namely the pole as well as the armature.




The Current supply will divided into two ways like  $I_a$  and  $I_{sh}$  where  $I_a$  will supply throughout the ' $R_a$ ' resistance armature winding. In the same ways ' $I_{sh}$ ' will supply through the ' $R_{sh}$ ' resistance field winding.

$$I_t = I_a + I_{sh} \quad \text{where } I_{sh} = \frac{E}{R_{sh}}$$

When

$$I_a = I_t - I_{sh} = \frac{E}{R_a}$$

Teacher's Signature : \_\_\_\_\_

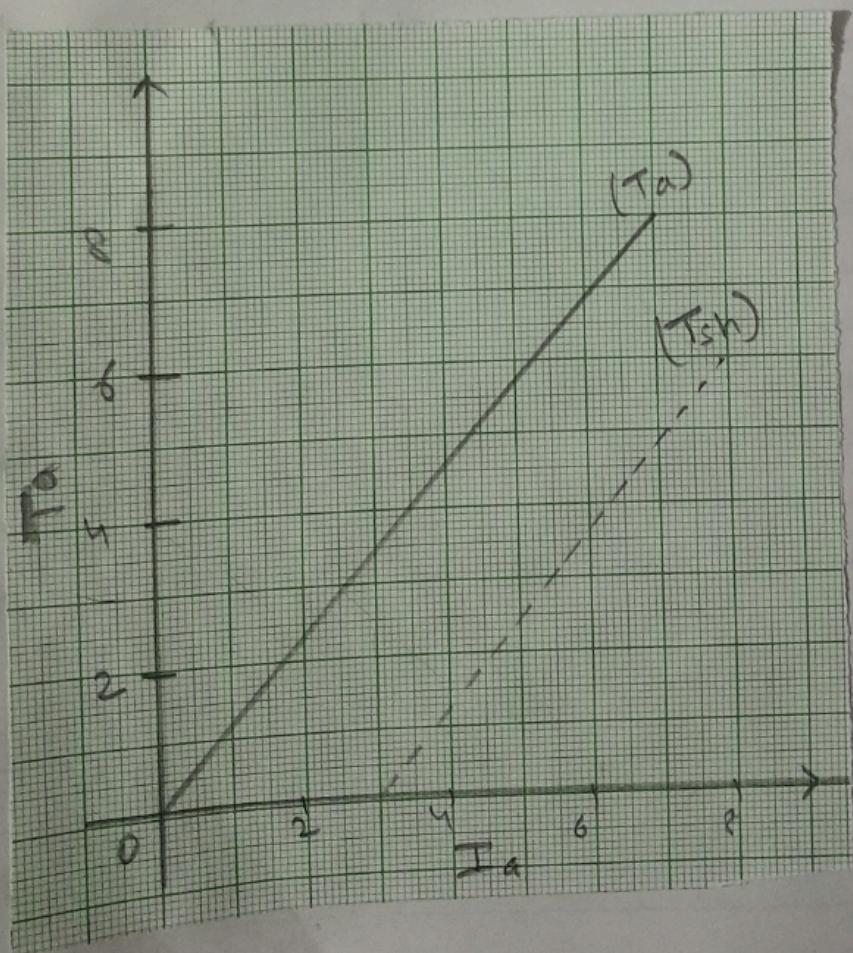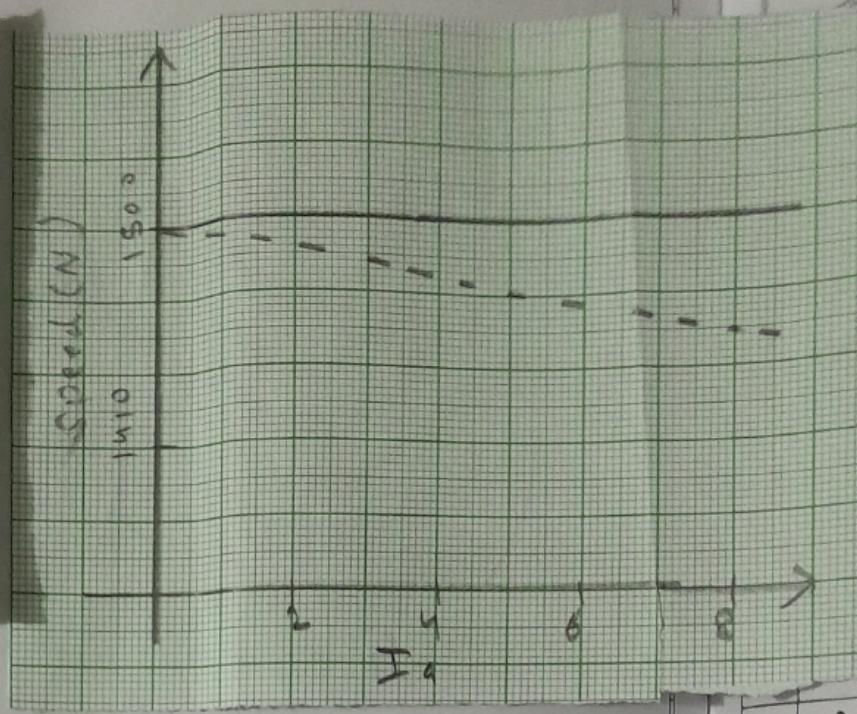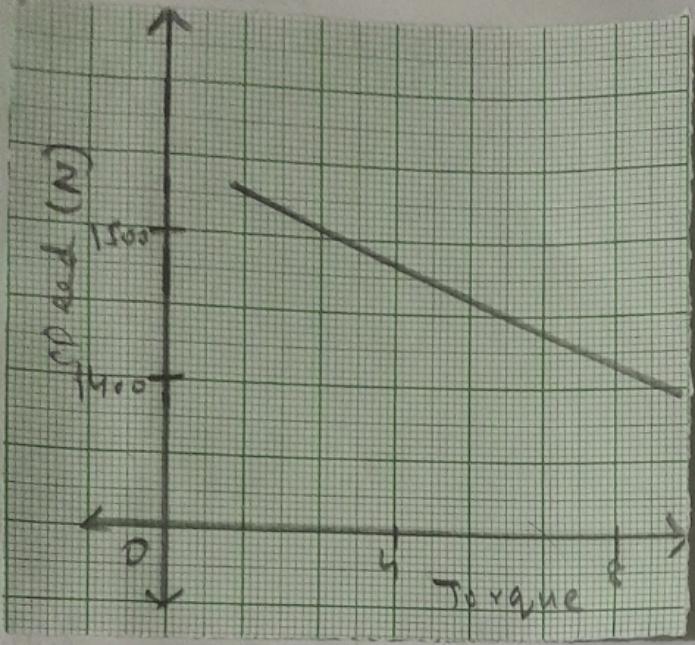

Re

The  
dr

Preco

Expt. No. \_\_\_\_\_

and emf

$$E_b = \frac{P \phi N z}{60 A}$$

here,

 $P \rightarrow$  no. of poles $\phi \rightarrow$  flux of each pole with  $\Theta_b$  $N \rightarrow$  motor speed (rpm) $A \rightarrow$  no. of parallel arms $z \rightarrow$  no. of armature conductors.Result

The characteristics of DC shunt motor is successfully drawn.

Precautions

- Speed should not exceed max. limit.
- Turn the field off by switching off the AC power to the field power. Field on first, field off last.


Teacher's Signature : \_\_\_\_\_

Aim  
To

Equipm  
Amm  
2 B

Theory  
A sin  
operat  
electric  
circuit  
induct

du  
he  
ci

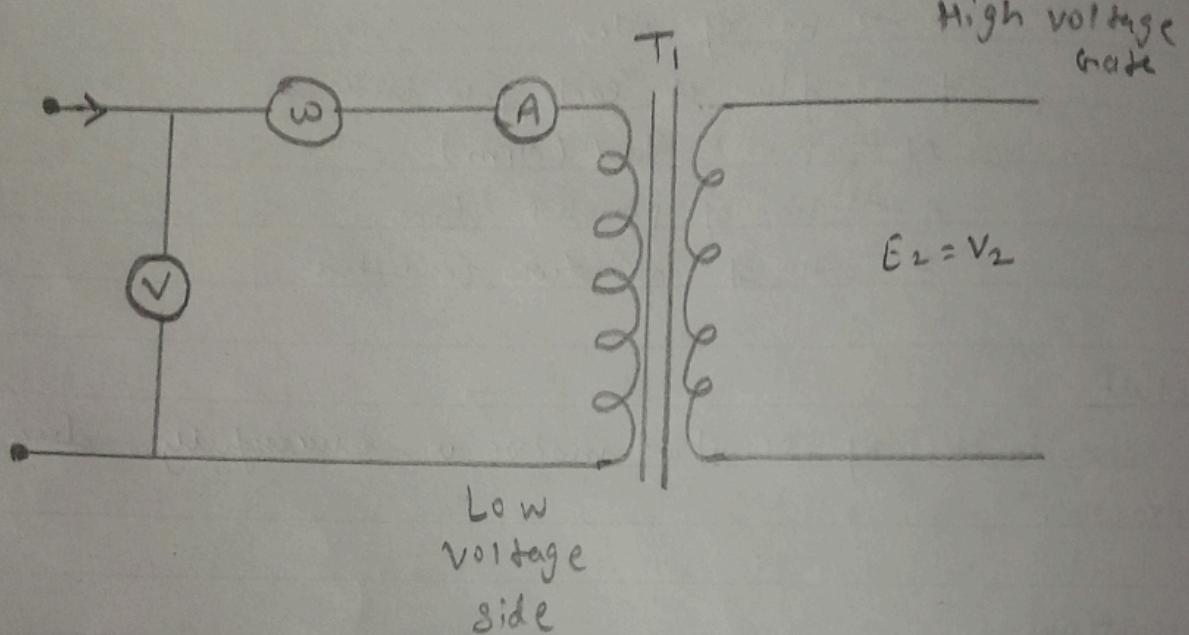

Practical - 4Aim

To Study open circuit test on Single phase transformer.

Equipment Required

Ammeter, Voltmeter, wattmeter, single phase transformer &  
~~& B.P.T.~~ D.P.T.

Theory

A single phase transformer is a type of transformer which operate on single phase power. A transformer is a passive electrical device that transfer electrical energy from one circuit to another through the process of electromagnetic induction.



- $V_o$  (No load primary voltage)
- $I_o$  (No load primary current)

$\omega_o$  -  ~~$\omega_o$~~  [load losses [core losses]]

due to small  $I_o$ , Copper losses will be very small.  
 hence we can't measure Copper losses from open circuit test

$$\omega_o = I_o V_o \cos \phi_o$$

$$\phi_o = \cos + \left( \frac{\omega_o}{I_o V_o} \right)$$

Teacher's Signature : \_\_\_\_\_

Date \_\_\_\_\_

Expt. No. \_\_\_\_\_

Page No. 8

$$I_C = I_0 \cos \phi_0, \quad I_M = I_0 \sin \phi_0$$

$$R_C = R_0 = \frac{V_U}{I_C}$$


$$X_M = X_0 = \frac{V_U}{I_M}$$

### Results

Test on open circuit single phase transformer verified.
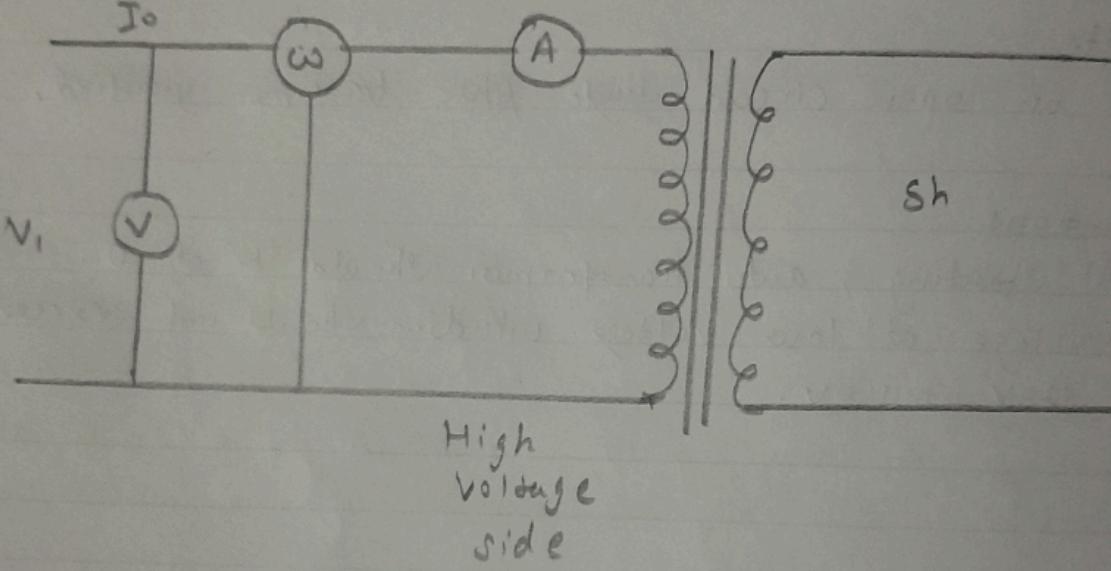
### Precautions

- At starting, auto transformer should be at 0.
- Voltage at low voltage winding should not exceed 120V or 110V.



Resu  
Test

Expt N

### Practical - 5

#### Aim

To Study short circuit test on single phase transformer.

#### Equipment Required

Wattmeter, Ammeter, Voltmeter, single phase transformer, and auto transformer.

#### Theory

It is performed to measure copper losses in a transformer normally performed on high voltage winding short circuiting low voltage windings.

Wattmeter will read copper losses, because of high current passing through windings.

$$W_{sc} = I_{sc}^2 \cdot R_{2e}$$



$$R_{2e} = \frac{W_{sc}}{I_{sc}^2}$$

$$Z_{2e} = \frac{V_{sc}}{I_{sc}}$$

$$X_{2e} = \sqrt{Z_{2e}^2 - R_{2e}^2}$$
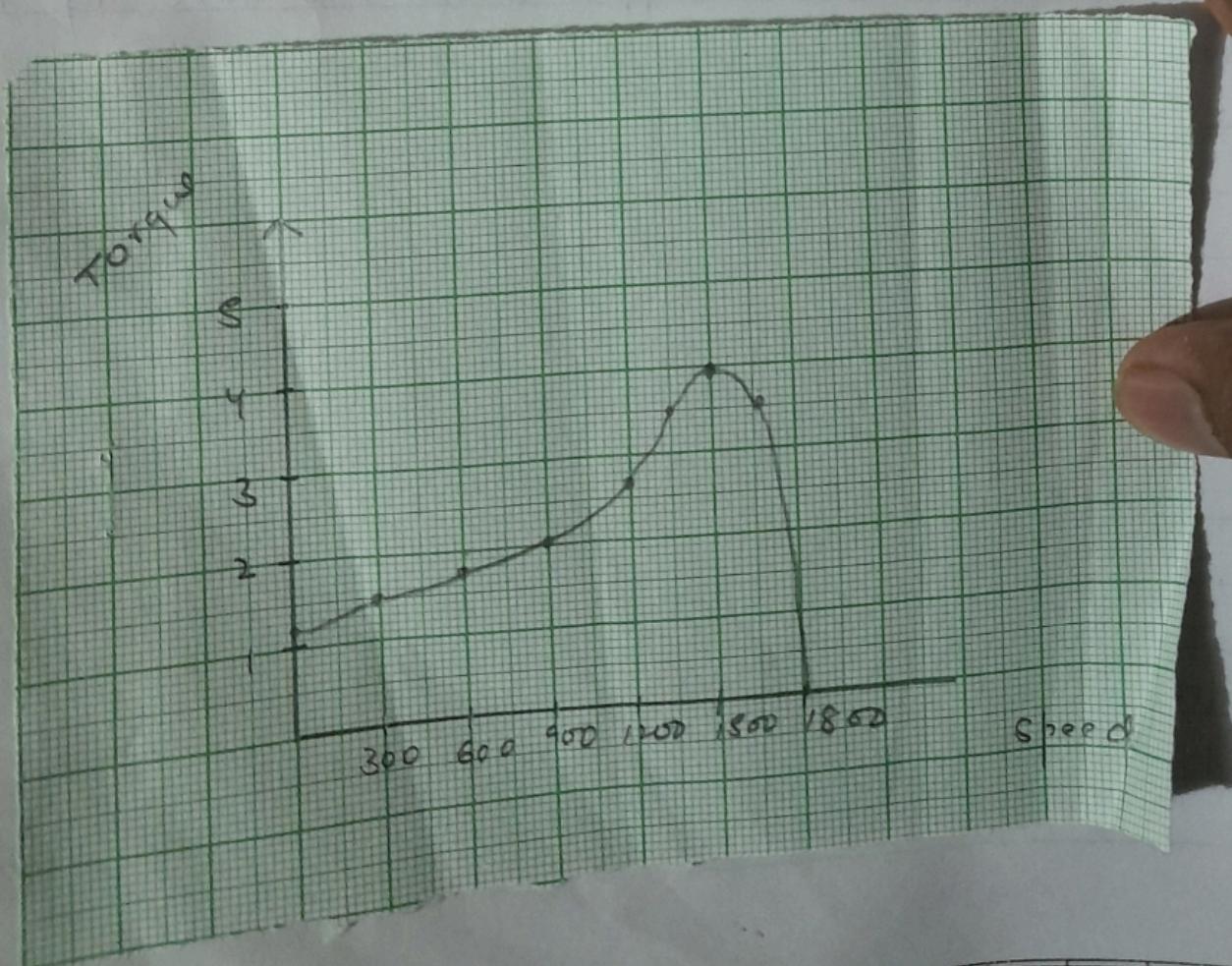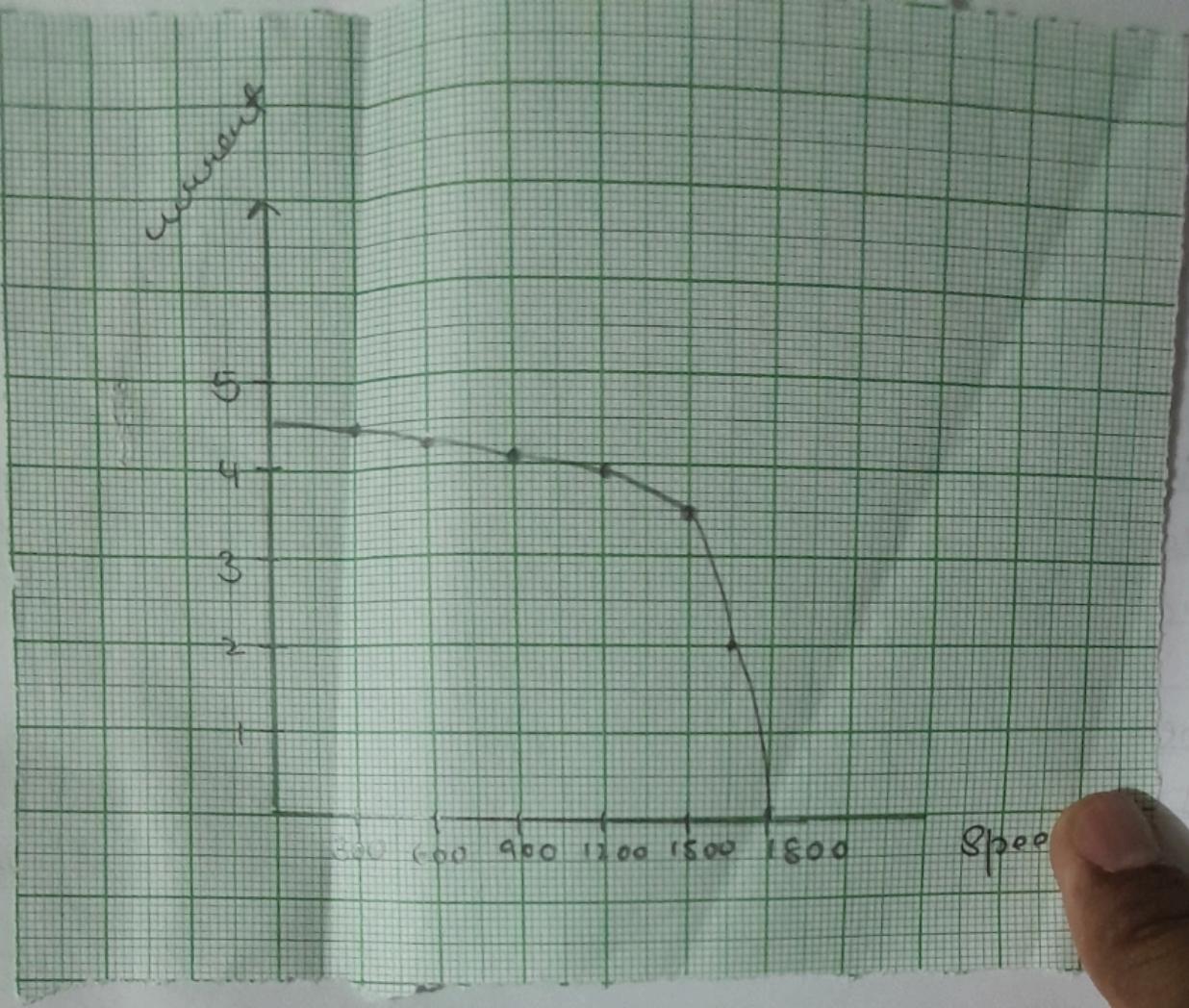
#### Result


Test on short circuit single phase transformer verified.




### Precautions

- Power should be disconnected before connecting the transformer to the apparatus
- Keep transformer away from magnetic objects
- Monitor the transformer temperature carefully.

## DC motor Control circuit

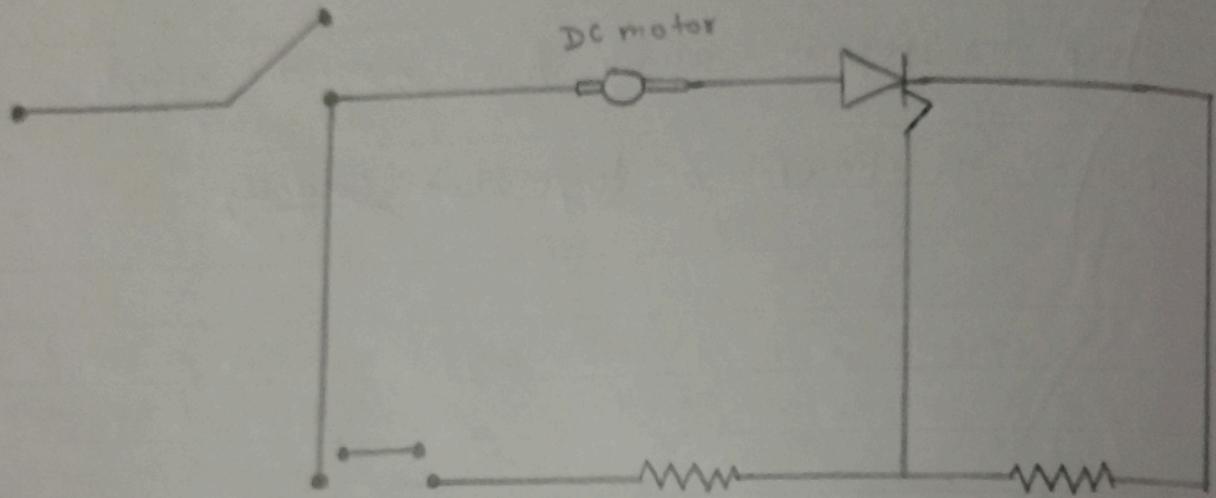

Anode

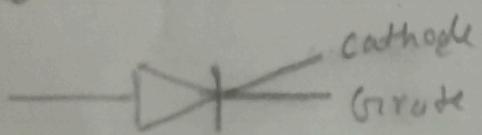

## Practical - 6

### Aim

Study the Control of DC motor using SCR.

### Equipment Required

DC motor, oscilloscope, BNC cable & multimeter.

### Theory

Silicon Controlled Rectifiers is a four-layered semiconductor device that conducts current in only one direction. It acts as a bidirectional switch and only conducts when gate arrives a current to trigger it once the SCR is triggered it remains in a conduction state until we reset it manually.


SCR switching circuit can be used to control much larger loads such as Sample lamps, motor etc.

In this practical, we will show how to control a DC motor by using SCR. The motor will start when we will apply pulse to its gate terminal.


### Precautions

- Check the connection properly before switching on the power.
- Keep transformer away from magnetic object



Armature current socket switch

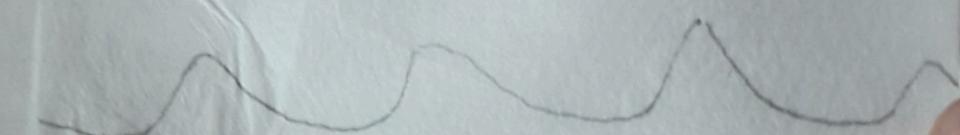

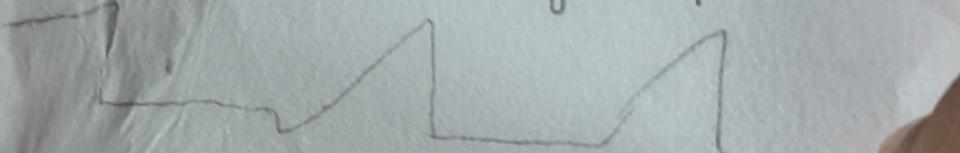Across SCR socket +ve, 1:10  
across var +1:16 of socket 4



Input +ve (SCR anode)

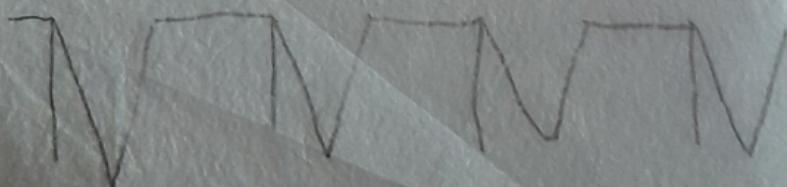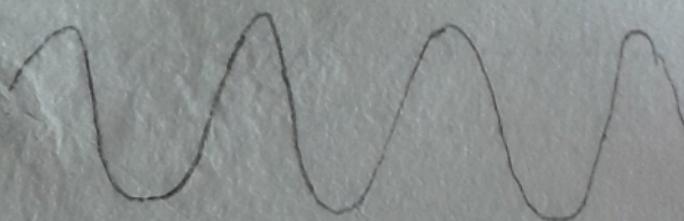

Socket +z (west)

Expt. No. \_\_\_\_\_

Date \_\_\_\_\_

Page.No. 12

- Monitor the transformer temperature Carefully

Result

Test on short circuit single phase transformer Verified.